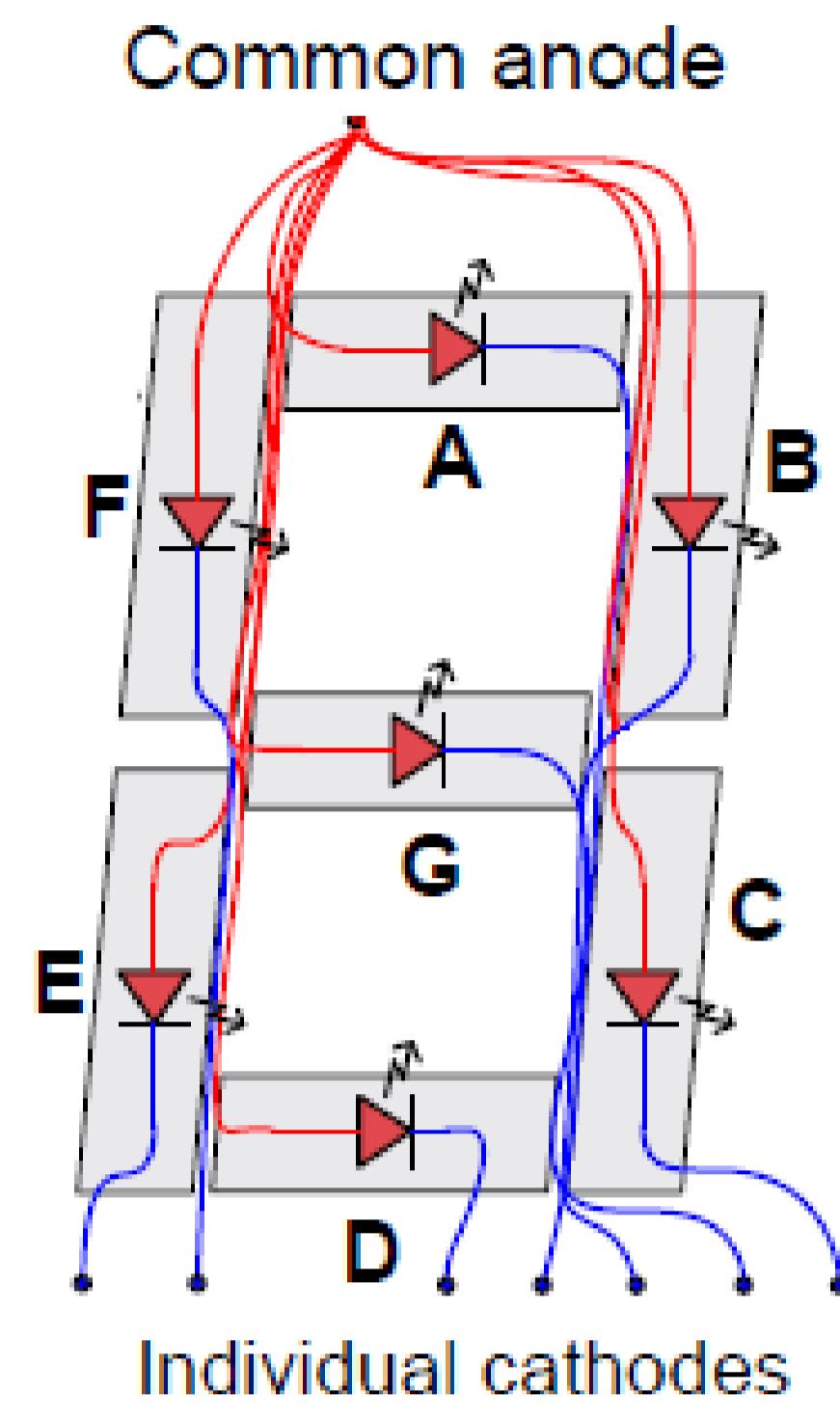


Problem 1

I3	I2	I1	I0	A	B	C	D	E	F	G
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1	1	0	0
1	0	1	0	0	0	0	1	0	0	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	1	1	1	0	0	1	0
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0



1. Fill the truth table for an active low seven segment decoder **Hint:** we will use lower case letters for 11, 12, 13 and upper case letters for 10, 14, and 15.
2. Using four variable K-maps find the most simplified minterms expressions for LEDs A to D.
3. Using four variable K-maps find the most simplified maxterms expressions for LEDs E to G.

Problem 2

1. Repeat problem 1 assuming BCD input which limits the digits between 0 and 9 and the rest are don't care.
2. Comment on how much the "don't care" inputs helped you to reduce your expressions.

Many of expressions were reduced by a lot, while a few were minimally reduced. Overall, setting our 7-segment to display to only numbers 0-9 (BCD) made our expressions more concise and therefore made our full logic circuit simpler.

Homework 4

Problem 1

2)

	$I_3 I_2$	$\cancel{I_1 I_0}$	$\cancel{\bar{I}_2 \bar{I}_1}$	$\cancel{\bar{I}_3 \bar{I}_2}$	$\cancel{I_0 \bar{I}_2}$	$\cancel{I_3 \bar{I}_2}$
$\bar{I}_1 \bar{I}_0$	00	01	10	11	10	00
$\bar{I}_1 I_0$	01	10	00	01	00	10
$I_1 \bar{I}_0$	11	10	01	00	01	11
$I_1 I_0$	10	00	11	00	10	00

$$A = \bar{I}_2 \bar{I}_0 + I_0 I_3 + \bar{I}_1 I_3 + I_2 \bar{I}_1 I_0 + \bar{I}_3 I_1 I_0$$

$$A = (I_2 + I_0)(I_0 + \bar{I}_3)(I_1 + I_3)(\bar{I}_2 + I_1 + \bar{I}_0)(I_3 + \bar{I}_1 + I_0)$$

	wx	$\bar{w}\bar{x}$	$\bar{w}x$	$w\bar{x}$	$w\bar{x}$
$\bar{y}\bar{z}$	00	01	11	10	00
$\bar{y}z$	01	00	01	10	00
$y\bar{z}$	11	10	01	11	10
$y\bar{z}$	10	00	11	00	10

It's suck, so...

$W = I_3$	$/ \text{ hope}$
$X = I_2$	
$Y = I_1$	
$Z = I_0$	

this helps

$$B = \bar{y}\bar{z} + \bar{x}\bar{z} + \bar{w}\bar{x}\bar{y} + w\bar{x}\bar{y} + \bar{w}xy$$

$$B = (y+z)(x+z)(w+x+y)(\bar{w}+\bar{x}+y)(w+\bar{x}+y)$$

	wx	$\bar{w}\bar{x}$	$\bar{w}x$	$w\bar{x}$	$w\bar{x}$
$\bar{y}\bar{z}$	00	01	11	10	00
$\bar{y}z$	01	00	00	00	00
$y\bar{z}$	11	10	01	11	10
$y\bar{z}$	10	00	00	00	00

$$C = \bar{y}\bar{z} + y\bar{z} + \bar{w}x + \bar{y}x + \bar{y}\bar{w}$$

$$C = (y+z)(\bar{y}+z)(w+x)(y+\bar{x})(\bar{y}+w)$$

WX	W	WX	W	X
YZ	00	01	11	10
YZ 00	0	1	0	0
YZ 01	1	0	1	0
YZ 11	0	0	1	0
YZ 10	0	1	0	1

$$D = \overline{W}\overline{X}Y + \overline{X}\overline{Y}\overline{Z} + \overline{W}X\overline{Z} + W\overline{X}\overline{Z} + WY\overline{Z} + W\overline{X}Z$$

$$D = (W+X+\overline{Y})(X+Y+Z)(W+X+Z)(\overline{W}+\overline{X}+Z)(\overline{W}+Y+Z)(\overline{W}+X+\overline{Z})$$

3)

WX	W	WX	W	X
YZ	00	01	11	10
YZ 00	0	1	1	0
YZ 01	1	1	1	0
YZ 11	0	0	0	0
YZ 10	0	1	0	0

$$E = X\overline{Y} + W\overline{Y}Z + \overline{W}X\overline{Z}$$

WX	W	WX	W	X
YZ	00	01	11	10
YZ 00	0	1	1	1
YZ 01	0	0	1	0
YZ 11	1	1	0	0
YZ 10	0	0	0	0

$$F = \overline{W}YZ + X\overline{Y}\overline{Z} + W\overline{Y}\overline{Z} + WX\overline{Y}$$

WX	W	WX	W	X
YZ	00	01	11	10
YZ 00	1	1	0	0
YZ 01	0	0	1	0
YZ 11	0	0	0	0
YZ 10	0	0	0	0

$$G = \overline{W}\overline{Y}\overline{Z} + W\overline{Y}Z$$

Problem 2

	wx	$\bar{w}\bar{x}$	$\bar{w}x$	$w\bar{x}$	$w\bar{x}$
yz	00	01	11	10	
$\bar{y}\bar{z}$	00	01	10	11	
$y\bar{z}$	01	10	00	01	
$y\bar{z}$	11	X	X	X	X
$y\bar{z}10$	00	01	X	X	

$$A = w + y + xz + \bar{x}\bar{z}$$

$$A = (\bar{w})(\bar{y})(\bar{x} + \bar{z})(x + z)$$

	wx	$\bar{w}\bar{x}$	$\bar{w}x$	$w\bar{x}$	$w\bar{x}$
yz	00	01	11	10	
$\bar{y}\bar{z}00$	00	01	10	11	
$\bar{y}\bar{z}01$	00	01	10	11	
$y\bar{z}11$	X	X	X	X	X
$y\bar{z}10$	00	01	X	X	X

$$B = y + \bar{z} + \bar{w}\bar{x} + w\bar{x}$$

$$B = (\bar{y})(z)(w+x)(\bar{w}+\bar{x})$$

	wx	$\bar{w}\bar{x}$	$\bar{w}x$	$w\bar{x}$	$w\bar{x}$
yz	00	01	11	10	
$\bar{y}\bar{z}00$	00	01	10	11	
$\bar{y}\bar{z}01$	00	01	00	00	
$y\bar{z}11$	X	X	X	X	X
$y\bar{z}10$	00	01	X	X	X

$$C = \bar{w} + x + z + y$$

$$C = (w)(\bar{x})(\bar{z})(\bar{y})$$

WZ	$\bar{W}X$	$\bar{W}X$	WX	WX
$\bar{Y}Z$	00	00	01	11
$\bar{Y}Z$	00	01	10	10
$\bar{Y}Z$	11	11	X X	X X
$\bar{Y}Z$	10	01	1 X	X 0

$$D = W\bar{X} + \bar{X}\bar{Z} + \bar{W}XZ + W\bar{Y}\bar{Z}$$

$$D = (\bar{W}+X)(X+Z)(W+\bar{X}+\bar{Z})(\bar{W}+Y+Z)$$

WZ	$\bar{W}X$	$\bar{W}X$	WX	WX
$\bar{Y}Z$	00	00	01	11
$\bar{Y}Z$	00	01	10	10
$\bar{Y}Z$	11	X X	X X	X X
$\bar{Y}Z$	10	01	X X	X X

$$E = X + \bar{W}Z$$

WZ	$\bar{W}X$	$\bar{W}X$	WX	WX
$\bar{Y}Z$	00	00	01	11
$\bar{Y}Z$	00	01	10	10
$\bar{Y}Z$	11	X X	X X	X X
$\bar{Y}Z$	10	01	X X	X X

$$F = WY + WX + XY\bar{Z}$$

WZ	$\bar{W}X$	$\bar{W}X$	WX	WX
$\bar{Y}Z$	00	00	01	11
$\bar{Y}Z$	00	01	10	10
$\bar{Y}Z$	11	X X	X X	X X
$\bar{Y}Z$	10	01	X X	X X

$$G = \bar{W}\bar{Y}\bar{Z} + WXZ$$